

# **INTRODUCTION TO MECHATRONICS AND MEASUREMENT SYSTEMS**

**2nd edition**

## **SOLUTIONS MANUAL**

**David G. Alciatore  
and  
Michael B. Hestand**

*Department of Mechanical Engineering  
Colorado State University  
Fort Collins, CO 80523*

## Solutions Manual

This manual contains solutions to the end-of-chapter problems in the second edition of "Introduction to Mechatronics and Measurement Systems." Only a few of the open-ended problems that do not have a unique answer are left for your creative solutions. More information, including an example course outline, a suggested laboratory syllabus, MathCAD files for examples in the book, and other supplemental material are provided on the Internet at:

<http://www.engr.colostate.edu/~dga/mechatronics.html>

We have class-tested the textbook for several years, and it should be relatively free from errors. However, if you notice any errors or have suggestions or advice concerning the textbook's content or approach, please feel free to contact us via e-mail at [dga@engr.colostate.edu](mailto:dga@engr.colostate.edu). We will post corrections for reported errors on our Web site.

Thank you for choosing our book. We hope it helps you provide your students with an enjoyable and fruitful learning experience in the cross-disciplinary subject of mechatronics.

## Solutions Manual

2.1  $D = 0.06408 \text{ in} = 0.001628 \text{ m}$ .

$$A = \frac{\pi D^2}{4} = 2.082 \times 10^{-6}$$

$$\rho = 1.7 \times 10^{-8} \Omega\text{m}, \quad L = 1000 \text{ m}$$

$$R = \frac{\rho L}{A} = 8.2 \Omega$$

2.2

(a)  $R_1 = 21 \times 10^4 \pm 20\%$  so  $168\text{k}\Omega \leq R_1 \leq 252\text{k}\Omega$

(b)  $R_2 = 07 \times 10^3 \pm 20\%$  so  $5.6\text{k}\Omega \leq R_2 \leq 8.4\text{k}\Omega$

(c)  $R_s = R_1 + R_2 = 217\text{k}\Omega \pm 20\%$  so  $174\text{k}\Omega \leq R_s \leq 260\text{k}\Omega$

(d)  $R_p = \frac{R_1 R_2}{R_1 + R_2}$

$$R_{p\text{MIN}} = \frac{R_{1\text{MIN}} R_{2\text{MIN}}}{R_{1\text{MIN}} + R_{2\text{MIN}}} = 5.43\text{k}\Omega$$

$$R_{p\text{MAX}} = \frac{R_{1\text{MAX}} R_{2\text{MAX}}}{R_{1\text{MAX}} + R_{2\text{MAX}}} = 8.14\text{k}\Omega$$

2.3  $R_1 = 10 \times 10^2$ ,  $R_2 = 25 \times 10^1$

$$R = \frac{R_1 R_2}{R_1 + R_2} = \frac{(10 \times 10^2)(25 \times 10^1)}{10 \times 10^2 + 25 \times 10^1} = 20 \times 10^1$$

a = 2 = red, b = 0 = black, c = 1 = brown, d = gold

2.4 In series, the trim pot will add an adjustable value ranging from 0 to its maximum value to the original resistor value depending on the trim setting. When in parallel, the trim pot could be  $0\Omega$  perhaps causing a short. Furthermore, the trim value will not be additive with the fixed resistor.

2.5 No, as long as you are consistent in your application, you will obtain correct answers. If you assume the wrong current direction, the result will be negative.

2.6 Place two  $100\Omega$  resistors in parallel and you immediately have a  $50\Omega$  resistance.

## Solutions Manual

2.7 From KCL,  $I_s = I_1 + I_2 + I_3$

so from Ohm's Law  $\frac{V_s}{R_{eq}} = \frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_3}$

Therefore,  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$  so  $R_{eq} = \frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}$

2.8 From Ohm's Law and Question 2.7,  $V = \frac{I_s}{R_{eq}} = \frac{I_s}{\frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}}$

and for one resistor,  $V = I_1 R_1$

Therefore,  $I_1 = \left( \frac{R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2} \right) I_s$

2.9  $\lim_{R_1 \rightarrow \infty} \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \frac{R_1 R_2}{R_1} = R_2$

2.10  $I = C_{eq} \frac{dV}{dt} = C_1 \frac{dV_1}{dt} = C_2 \frac{dV_2}{dt}$

From KVL,

$$V = V_1 + V_2$$

so

$$\frac{dV}{dt} = \frac{dV_1}{dt} + \frac{dV_2}{dt}$$

Therefore,

$$\frac{I}{C_{eq}} = \frac{I}{C_1} + \frac{I}{C_2} \text{ so } \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \text{ or } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

2.11  $V = V_1 = V_2$

$$I_1 = C_1 \frac{dV_1}{dt} = C_1 \frac{dV}{dt} \text{ and } I_2 = C_2 \frac{dV_2}{dt} = C_2 \frac{dV}{dt}$$

From KCL,

$$I = I_1 + I_2 = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} = \frac{dV}{dt} (C_1 + C_2)$$

## Solutions Manual

$$\text{Since } I = C_{\text{eq}} \frac{dV}{dt}$$

$$C_{\text{eq}} = C_1 + C_2$$

$$2.12 \quad I = I_1 = I_2$$

From KVL,

$$V = V_1 + V_2 = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} = \frac{dI}{dt} (L_1 + L_2)$$

$$\text{Since } V = L_{\text{eq}} \frac{dI}{dt}$$

$$L_{\text{eq}} = L_1 + L_2$$

$$2.13 \quad V = L \frac{dI}{dt} = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt}$$

$$\text{From KCL, } I = I_1 + I_2 \quad \text{so} \quad \frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$\text{Therefore, } \frac{V}{L} = \frac{V}{L_1} + \frac{V}{L_2} \quad \text{so} \quad \frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} \quad \text{or} \quad L = \frac{L_1 L_2}{L_1 + L_2}$$

$$2.14 \quad V_o = 1 \text{ V, regardless of the resistance value.}$$

$$2.15 \quad \text{From Voltage Division, } V_o = \frac{40}{10 + 40} (5 - 15) = -8 \text{ V}$$

$$2.16 \quad \text{Combining } R_2 \text{ and } R_3 \text{ in parallel,}$$

$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = \frac{2(3)}{2 + 3} = 1.2 \text{ k}$$

and combining this with  $R_1$  in series,

$$R_{123} = R_1 + R_{23} = 2.2 \text{ k}$$

(a) Using Ohm's Law,

$$I_1 = \frac{V_{\text{in}}}{R_{123}} = \frac{5 \text{ V}}{2.2 \text{ k}} = 2.27 \text{ mA}$$

## Solutions Manual

(b) Using current division,

$$I_3 = \frac{R_2}{R_2 + R_3} I_1 = \frac{2}{5} 2.27 \text{mA} = 0.909 \text{mA}$$

(c) Since  $R_2$  and  $R_3$  are in parallel, and since  $V_{\text{in}}$  divides between  $R_1$  and  $R_{23}$ ,

$$V_3 = V_{23} = \frac{R_{23}}{R_1 + R_{23}} V_{\text{in}} = \frac{1.2}{2.2} 5 \text{V} = 2.73 \text{V}$$

2.17

(a) From Ohm's Law,

$$I_4 = \frac{V_{\text{out}} - V_1}{R_{24}} = \frac{14.2 \text{V} - 10 \text{V}}{6 \text{k}} = 0.7 \text{mA}$$

(b)  $V_5 = V_6 = V_{56} = V_{\text{out}} - V_2 = 14.2 \text{V} - 20 \text{V} = -5.8 \text{V}$

2.18

(a)  $R_{45} = R_4 + R_5 = 3 \text{k}\Omega$

$$R_{345} = \frac{R_3 R_{45}}{R_3 + R_{45}} = 1.5 \text{k}\Omega$$

$$R_{2345} = R_2 + R_{345} = 3.5 \text{k}\Omega$$

$$R_{\text{eq}} = \frac{R_1 R_{2345}}{R_1 + R_{2345}} = 0.778 \text{k}\Omega$$

(b)  $V_A = \frac{R_{345}}{R_2 + R_{345}} V_s = 4.29 \text{V}$

(c)  $I_{345} = \frac{V_A}{R_{345}} = 2.86 \text{mA}$

$$I_5 = \frac{R_3}{R_3 + R_{45}} I_{345} = 1.43 \text{mA}$$

2.19 Using superposition,

$$V_{R2_1} = \frac{R_2}{R_1 + R_2} V_1 = 0.909 \text{V}$$

## Solutions Manual

$$V_{R_{2_2}} = \frac{R_1}{R_1 + R_2} i_1 = 9.09\text{V}$$

$$V_{R_2} = V_{R_{2_1}} + V_{R_{2_2}} = 10.0\text{V}$$

$$2.20 \quad R_{45} = \frac{R_4 R_5}{R_4 + R_5} = 0.5\text{k}\Omega$$

$$I = \frac{V_1 - V_2}{R_1 + R_2} = -0.5\text{mA}$$

$$V_A = \frac{R_{45}}{R_3 + R_{45}} (V_1 - V_2) = -0.238\text{V}$$

2.21 It will depend on your instrumentation, but the oscilloscope typically has an input impedance of  $1\text{ M}\Omega$ .

2.22 Since the input impedance of the oscilloscope is  $1\text{ M}\Omega$ , the impedance of the source will be in parallel, and the oscilloscope impedance will affect the measured voltage. Draw a sketch of the equivalent circuit to convince yourself.

$$2.23 \quad R_{23} = \frac{R_2 R_3}{R_2 + R_3}$$

$$V_{\text{out}} = \frac{R_{23}}{R_3 + R_{23}} V_{\text{in}}$$

$$(a) \quad R_{23} = 9.90\text{k}\Omega, \quad V_{\text{out}} = 0.995 V_{\text{in}}$$

$$(b) \quad R_{23} = 333\text{k}\Omega, \quad V_{\text{out}} = 1.00 V_{\text{in}}$$

When the impedance of the load is lower ( $10\text{k}$  vs.  $500\text{k}$ ), the accuracy is not as good.

2.24 It will depend on the supply; check the specifications before answering.

$$2.25 \quad V_{\text{in}} = 5\angle 45^\circ$$

Combining  $R_2$  and  $L$  in series and the result in parallel with  $C$  gives:

$$Z_{R_2LC} = \frac{(R_2 + Z_L)Z_C}{(R_2 + Z_L) + Z_C} = 1860.52\angle -60.25^\circ = 923.22 - 1615.30j$$

## Solutions Manual

Using voltage division,

$$V_C = \frac{Z_{R_2LC}}{R_1 + Z_{R_2LC}} V_{in}$$

where

$$R_1 + Z_{R_2LC} = 1000 + 923.22 - 1615.30j = 2511.57 \angle -40.02^\circ$$

so

$$V_C = \frac{1860.52 \angle -60.25^\circ}{2511.57 \angle -40.02^\circ} 5 \angle 45^\circ = 3.70 \angle 24.8^\circ = 3.70 \angle 0.433 \text{ rad}$$

Therefore,

$$V_C(t) = 3.70 \cos(3000t + 0.433) \text{ V}$$

2.26 With steady state dc  $V_s$ , C is open circuit. So

$$V_C = V_s = 10 \text{ V} \text{ so } V_{R_1} = 0 \text{ V} \text{ and } V_{R_2} = V_s = 10 \text{ V}$$

2.27

(a) In steady state dc, C is open circuit and L is short circuit. So

$$I = \frac{V_s}{R_1 + R_2} = 0.025 \text{ mA}$$

(b)  $\omega = \pi$

$$Z_C = \frac{-j}{\omega C} = \frac{10^6}{\pi} j = \frac{10^6}{\pi} \angle -90^\circ \Omega$$

$$Z_{LR_2} = Z_L + R_2 = j\omega L + R_2 = (10^5 + 20\pi j) \Omega = 10^5 \angle 0.036^\circ \Omega$$

$$Z_{CLR_2} = \frac{Z_C Z_{LR_2}}{Z_C + Z_{LR_2}} = (91040 - 28550j) \Omega = 95410 \angle -17.4^\circ \Omega$$

$$Z_{eq} = R_1 + Z_{CLR_2} = (191040 - 28550j) \Omega = 193200 \angle -8.50^\circ \Omega$$

$$I_s = \frac{V_s}{Z_{eq}} = 0.0259 \angle 8.50^\circ \text{ mA}$$

$$I = \frac{Z_C}{Z_C + Z_{LR_2}} I_s = (0.954 \angle -17.44^\circ) I_s = 0.0247 \angle -8.94^\circ \text{ mA}$$



## Solutions Manual

So

$$I(t) = 24.7 \cos(\pi t - 0.156) \mu\text{A}$$

2.28

$$(a) \quad \omega = \pi \frac{\text{rad}}{\text{sec}}, \quad f = \frac{\omega}{2\pi} = 0.5 \text{ Hz}$$

$$A_{\text{pp}} = 2A = 4.0, \quad \text{dc}_{\text{offset}} = 0$$

$$(b) \quad \omega = 2\pi \frac{\text{rad}}{\text{sec}}, \quad f = \frac{\omega}{2\pi} = 1 \text{ Hz}$$

$$A_{\text{pp}} = 2A = 2, \quad \text{dc}_{\text{offset}} = 10.0$$

$$(c) \quad \omega = 2\pi \frac{\text{rad}}{\text{sec}}, \quad f = \frac{\omega}{2\pi} = 1 \text{ Hz}$$

$$A_{\text{pp}} = 2A = 6.0, \quad \text{dc}_{\text{offset}} = 0$$

$$(d) \quad \omega = 0 \frac{\text{rad}}{\text{sec}}, \quad f = \frac{\omega}{2\pi} = 0 \text{ Hz}$$

$$A_{\text{pp}} = 2A = 0, \quad \text{dc}_{\text{offset}} = \sin(\pi) + \cos(\pi) = -1$$

$$2.29 \quad P = \frac{V_{\text{rms}}^2}{R} = 100 \text{ W}$$

$$2.30 \quad V_{\text{rms}} = \left( \frac{V_{\text{pp}}}{2} \right) / (\sqrt{2}) = 35.36 \text{ V}$$

$$P = \frac{V_{\text{rms}}^2}{R} = 12.5 \text{ W}$$

$$2.31 \quad V_{\text{m}} = \sqrt{2} V_{\text{rms}} = 169.7 \text{ V}$$

$$2.32 \quad \text{For } V_{\text{rms}} = 120 \text{ V}, \quad V_{\text{m}} = \sqrt{2} V_{\text{rms}} = 169.7 \text{ V}, \quad \text{and } f = 60 \text{ Hz},$$

$$V(t) = V_{\text{m}} \sin(2\pi f t + \phi) = 169.7 \sin(120\pi t + \phi)$$

## Solutions Manual

2.33 From Ohm's Law,

$$I = \frac{5V - 2V}{R} = \frac{3V}{R}$$

Since  $10\text{mA} \leq I \leq 100\text{mA}$ ,

$$10\text{mA} \leq \frac{3V}{R} \leq 100\text{mA}$$

giving

$$\frac{3V}{100\text{mA}} \leq R \leq \frac{3V}{10\text{mA}} \quad \text{or} \quad 30\Omega \leq R \leq 300\Omega$$

For a resistor,  $P = \frac{V^2}{R}$ , so the smallest allowable resistance would need a power rating of at least:

$$P = \frac{(3V)^2}{30\Omega} = 0.3\text{W}$$

so a 1/2 W resistor should be specified.

The largest allowable resistance would need a power rating of at least:

$$P = \frac{(3V)^2}{300\Omega} = 0.03\text{W}$$

so a 1/4 W resistor would provide more than enough capacity.

2.34 Using KVL and KCL gives:

$$V_1 = I_{R_1} R_1$$

$$V_1 = (I_1 - I_{R_1})R_2 + (I_1 - I_{R_1} - I_2)R_3$$

$$V_3 - V_2 = (I_1 - I_{R_1} - I_2)R_3 - I_2 R_4$$

The first loop equation gives:

$$I_{R_1} = \frac{V_1}{R_1} = 10\text{mA}$$

Using this in the other two loop equations gives:

$$10 = (I_1 - 10\text{mA})2\text{k} + (I_1 - 10\text{mA} - I_2)3\text{k}$$

$$10 - 5 = (I_1 - 10\text{mA} - I_2)3\text{k} - I_2 4\text{k}$$

## Solutions Manual

or

$$(5k)I_1 - (3k)I_2 = 60$$

$$(3k)I_1 - (7k)I_2 = 35$$

Solving these equations gives:

$$I_1 = 12.12\text{mA} \text{ and } I_2 = 0.1923\text{mA}$$

$$(a) \quad V_{\text{out}} = I_2 R_4 - V_2 = -4.23\text{V}$$

$$(b) \quad P_1 = I_1 V_1 = 121\text{mW}, \quad P_2 = I_2 V_2 = 0.962\text{mW}, \quad P_3 = -I_2 V_3 = -1.92\text{mW}$$

2.35 Using KVL and KCL gives:

$$V_1 = I_{R_1} R_1$$

$$V_1 = (I_1 - I_{R_1})R_2 + (I_1 - I_{R_1} - I_2)R_3$$

$$V_3 - V_2 = (I_1 - I_{R_1} - I_2)R_3 - I_2 R_4$$

The first loop equation gives:

$$I_{R_1} = \frac{V_1}{R_1} = 10\text{mA}$$

Using this in the other two loop equations gives:

$$10 = (I_1 - 10\text{m})2k + (I_1 - 10\text{m} - I_2)2k$$

$$10 - 5 = (I_1 - 10\text{m} - I_2)2k - I_2 1k$$

or

$$(4k)I_1 - (2k)I_2 = 50$$

$$(2k)I_1 - (3k)I_2 = 25$$

Solving these equations gives:

$$I_1 = 12.5\text{mA} \text{ and } I_2 = 0\text{mA}$$

$$(a) \quad V_{\text{out}} = I_2 R_4 - V_2 = -5\text{V}$$

$$(b) \quad P_1 = I_1 V_1 = 125\text{mW}, \quad P_2 = I_2 V_2 = 0\text{mW}, \quad P_3 = -I_2 V_3 = 0\text{mW}$$

$$2.36 \quad P_{\text{avg}} = \frac{1}{T} \int_0^T V(t)I(t)dt = \frac{V_m I_m}{T} \int_0^T \sin(\omega t + \phi_V) \sin(\omega t + \phi_I) dt$$

## Solutions Manual

Using the product formula trigonometric identity,

$$P_{\text{avg}} = \frac{V_m I_m}{2T} \int_0^T (\cos(\phi_V - \phi_I) - \cos(2\omega t + \phi_V + \phi_I)) dt$$

Therefore,

$$P_{\text{avg}} = \frac{V_m I_m}{2} \cos(\phi_V - \phi_I) = \frac{V_m I_m}{2} \cos(\theta)$$

$$2.37 \quad I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \sin^2(\omega t + \phi_I) dt}$$

Using the double angle trigonometric identity,

$$I_{\text{rms}} = \sqrt{\frac{I_m^2}{T} \int_0^T \left( \frac{1}{2} - \cos[2(\omega t + \phi_I)] \right) dt}$$

Therefore,

$$I_{\text{rms}} = \sqrt{\frac{I_m^2}{T} \left( \frac{T}{2} \right)} = \frac{I_m}{2}$$

$$2.38 \quad R_{23} = \frac{R_2 R_3}{R_2 + R_3} = 5 \text{ k}\Omega$$

$$V_o = \frac{R_{23}}{R_1 + R_{23}} V_i = \frac{1}{2} \sin(2\pi t)$$

This is a sin wave with half the amplitude of the input with a period of 1s.

$$2.39 \quad \frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{120 \text{ V}}{24 \text{ V}} = 5$$

$$2.40 \quad R_L = R_i = 100 \Omega \text{ for maximum power}$$

2.41 The BNC cable is far more effective in shielding the input signals from electromagnetic interference since no loops are formed.